



This acts as a DC offset.  
 Remember that it has a gain set by the Q  $[(Rq1+Rq2)/Rq1]$ .

With a Q of 2 (10k,10k) to get 1 V offset at output we require a voltage of 0.5V